

Cuk converter

Thursday, March 11, 2021 9:17 AM

Motivation

- Synthesize a DC-DC circuit that can increase/decrease ϕ/p voltage.
- Both ϕ/p & ϕ/p currents non-pulsating or continuous.

Buck / Boost / Buck-boost


Gain of buck-boost = gain of buck \times gain of boost

$$\frac{D}{D'} = \underbrace{\left(D\right) \left(\frac{1}{D'}\right)}_{\text{cascaded design}}$$


CUK converter

→ ϕ/p stage = Boost

→ ϕ/p ' = Buck

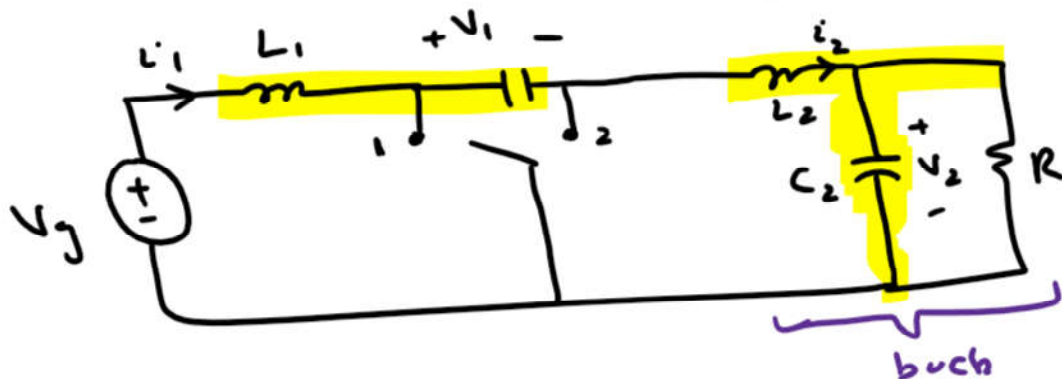

At position #1

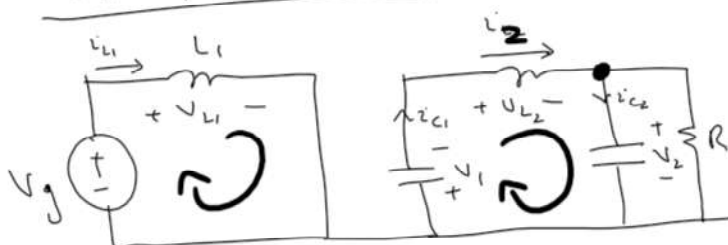

$$V_{L1} = V_g \quad \text{KVL}$$

$$V_{L2} = -V_1 - V_2 \quad \text{KVL}$$


$$i_{C1} = i_2 \quad \text{KCL}$$

$$\rightarrow i_{C2} = i_2 - \frac{V_2}{R} \quad \text{KCL}$$

small ripple approximation

$$V_{L1} = V_g$$

$$\underline{V_{L2} = -V_1 - V_2}$$

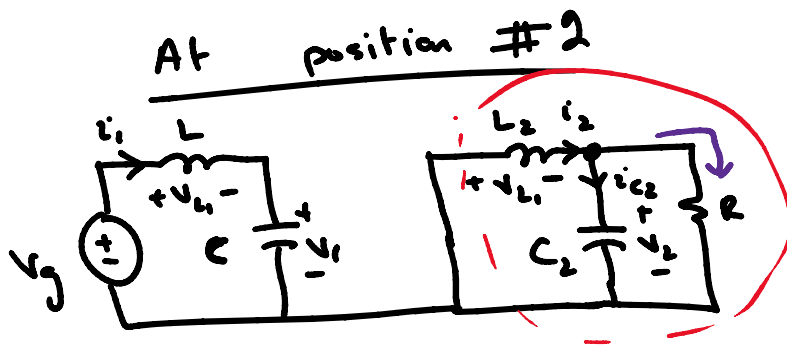

$$\begin{aligned} V_{L2} &= -V_1 - V_2 \\ i_{C1} &= I_2 \\ i_{C2} &= I_2 - \frac{V_2}{R} \end{aligned}$$

$$\begin{aligned} V_{L1} &= V_g - V_1 \\ V_{L2} &= -V_2 \\ i_{C1} &= i_1 \\ i_{C2} &= i_2 - \frac{V_2}{R} \end{aligned} \quad \left. \begin{array}{l} \text{KVL} \\ \text{KCL} \end{array} \right\}$$

Small ripple approximation.


$$V_{L1} = V_g - V_1$$

$$V_{L2} = -V_2$$

$$i_{C1} = I_1$$

$$i_{C2} = I_2 - \frac{V_2}{R}$$

Drawing the key waveforms

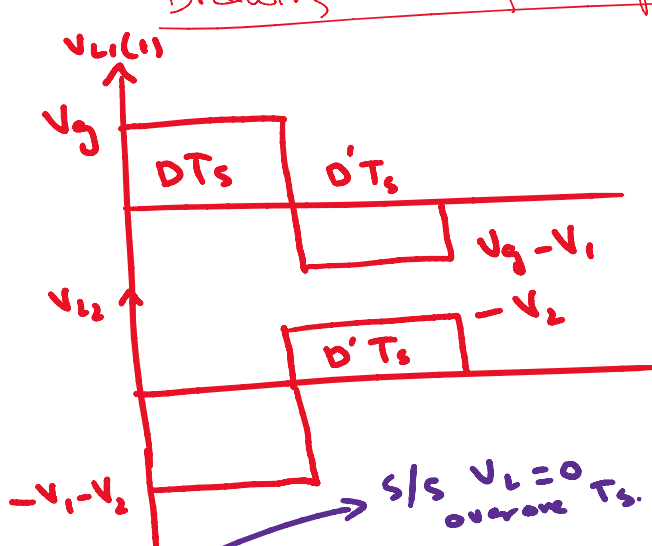


s/s $V_L = 0$ over one T_s .

$$\langle V_{L1} \rangle = 0 = V_g D + D' (V_g - V_1) = V_g / D'$$

$$\langle V_{L2} \rangle = 0 = D(-V_1 - V_2) + D'(-V_2)$$
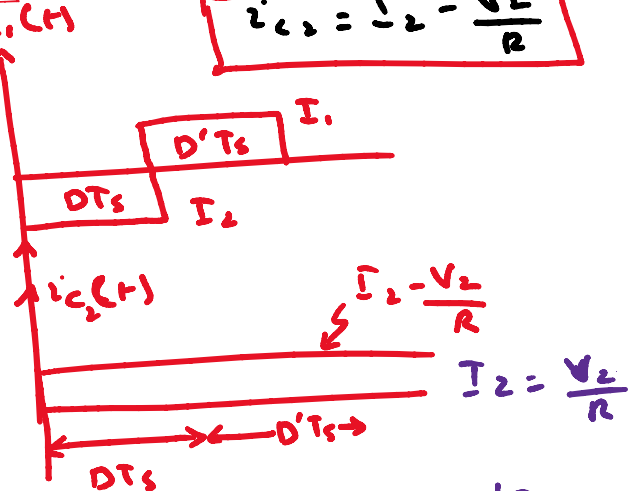
$$V_2 = \frac{D}{D'} V_g \quad \text{--- (A)}$$



$$\begin{aligned} \langle i_{C1} \rangle &= 0 = D I_2 + D' I_1 \\ I_1 &= \left(\frac{-D}{D'} \right) I_2 = \frac{-D}{D'} \frac{V_2}{R} \\ &= \left(\frac{D}{D'} \right)^2 \frac{V_g}{R} \end{aligned}$$

$$\langle i_{C2} \rangle = I_2 - \frac{V_2}{R} = 0$$


$$I_2 = \frac{D}{D'} \frac{V_g}{R}$$

$$M(D) = \frac{V_2}{V_g} = \frac{-D}{D'} = \frac{D}{1-D}$$




for V_g

$D > 0.5$	$V_2 > V_g$
$D < 0.5$	$V_2 < V_g$
$D = 0.5$	$V_2 = V_g$

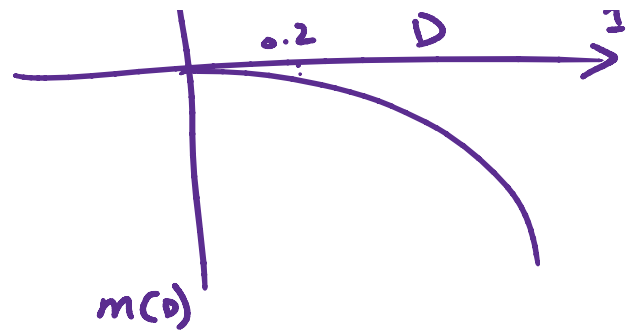

L_1 Expression based on i_{L1}

$$L_1 = \frac{V_g}{2 \Delta i_1} D T_s$$

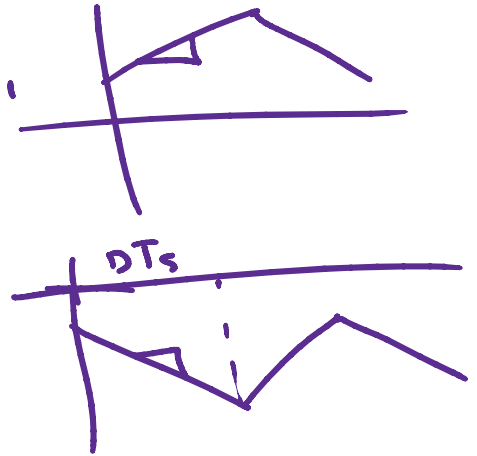


L_2 expression

$$L_2 = \frac{V_1 + V_2}{2 \Delta i_2} D T_s$$


C_1 expression

$$C_1 = \frac{I_2}{2 \Delta V_1} D T_s$$

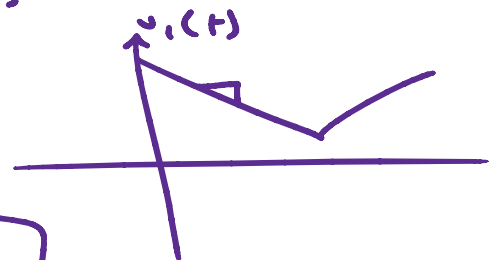

how to determine the C_2 .

→ $i_{C2}(t)$ is continuous.

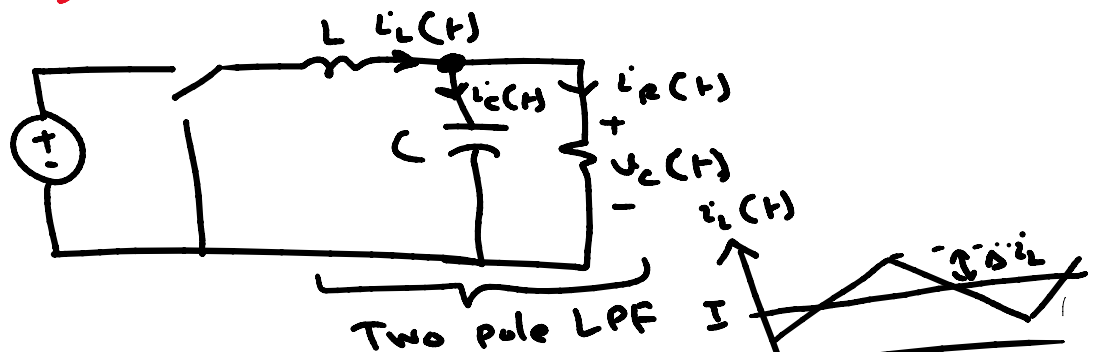

$$i_L(t) = I + \Delta i_L$$

— a. Low frequency

$$z_L(r) = \dots$$

DC component I can only flow through R
 b/c $X_C = \frac{1}{2\pi f_c} = \infty$ so I can't flow through C.




In a well designed converter

$$\text{if } Z_C > R \\ Z_C < R$$

$$X_C \ll R$$

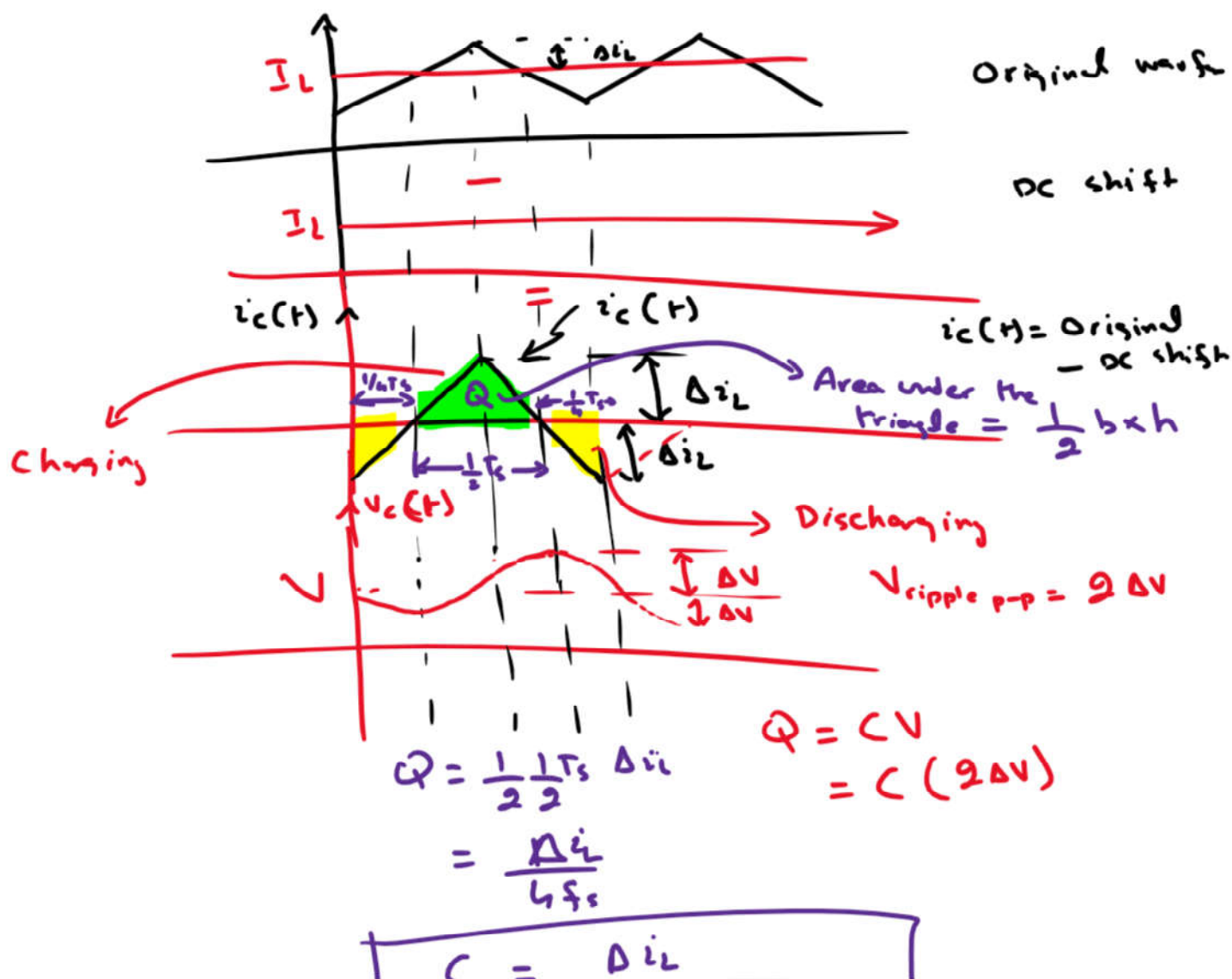To ensure this C is kept large $X_C = \frac{1}{2\pi f_c}$
 Ideally all Δi_L flows through 'C'




$$C = \frac{\Delta i_L}{8 f_s \Delta V}$$


Discussion

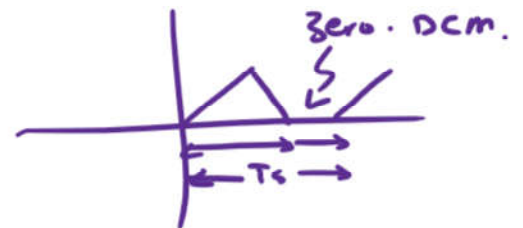- 1) All DC-DC are non-linear.
 ↳ subcircuits are linear ^{first order} [2nd order]
 but high freq switching changes their structure & its periodic structured change make the converter itself a non-linear circuit.

→ Add converter, $i_L > 0$ no this is called continuous conduction mode (CCM).



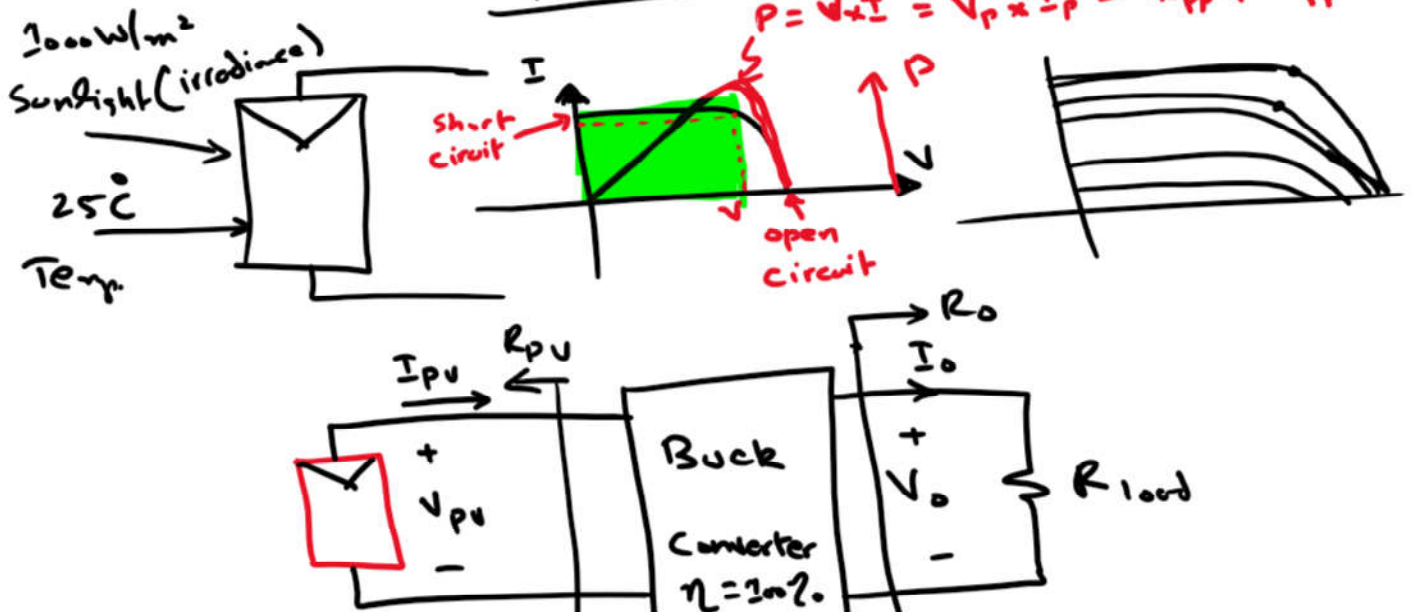Application of basic converter in photovoltaic system.








$$V_o = DV_{in}$$

$$V_o = DV_{pv}$$

$$P_{in} = P_o \quad I_o = I_{pv}/D$$
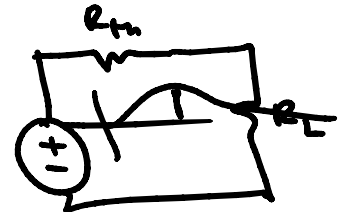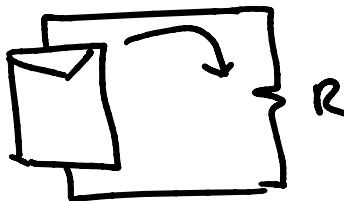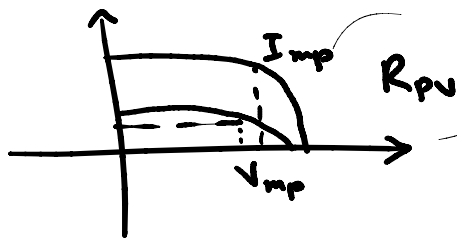
$$R_{pv} = \frac{V_{pv}}{I_{pv}} = \frac{V_o/D}{I_o D} = \frac{V_o}{I_o D^2} = \frac{R_o}{D^2} = \frac{R_{load}}{D^2}$$



$$R = R_{pv}$$

$$R_{pv} = \frac{R_{load}}{D^2}$$

$$\text{If } D = 1$$

$$D = 0$$

$$R_{pv} = R_{load}$$

$$R_{pv} = \infty$$

If

$$R_{load} > R_{pv}$$

buck converter can't match the impedance & hence can't transfer the MPP or it can't track mppt.

